

1. (Boolean function representation- 30 points) Consider a Boolean threshold function f_T that is equal to one if at least 3 out of its 4 input bits are one. Construct:
 - a) Truth table
 - b) Sum of products expression that is irredundant and prime
 - c) Binary Decision Tree
 - d) Binary Decision Diagram derived from c) representing the function f_T .


In deriving the above circuit representations, please refer to the steps taken, including the use of appropriate expansions (e.g, Shannon, Davio), as detailed out in the textbook.

2. (Pseudo-Boolean, or word-level representation – 20 points) Consider a word-level function over three words

$$f = a * b + c,$$

where a , b and c are n -bit unsigned integers.

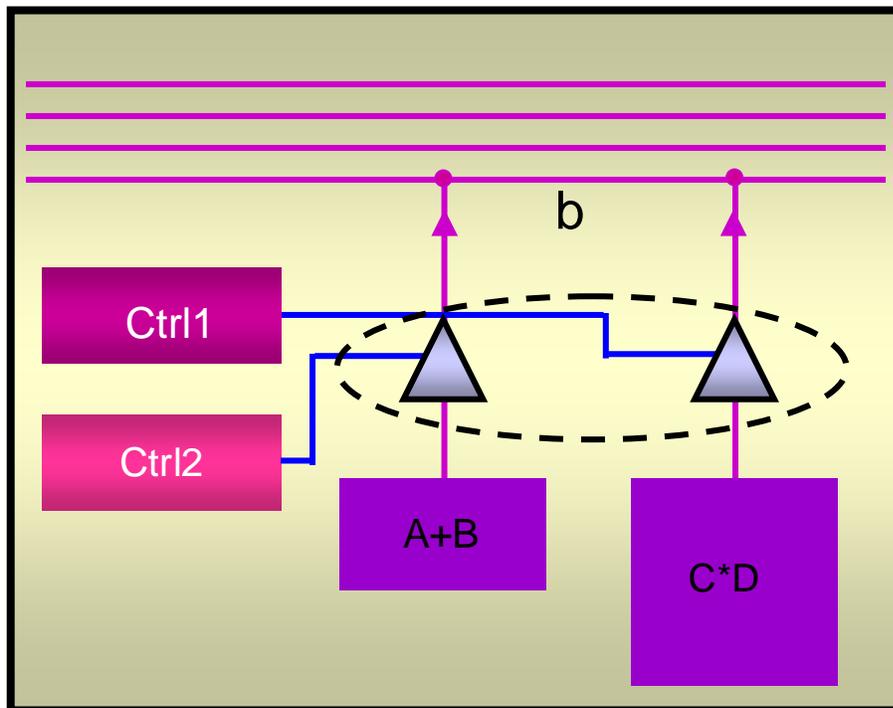- a) Construct its representation by a word-level polynomial, i.e. its Arithmetic Transform. Explain steps used in obtaining the polynomial from this description.
 - b) Show the polynomial describing multiplication in both expanded and unexpanded forms.
3. (Bus Errors – 30 points). Consider an adder and a multiplier connected to the common buses:



Assume that A and B are 4-bit unsigned integers, while C and D are 3-bit unsigned integers.

- a) Denote the width of the common (shared) bus b
 - b) Describe error type 8 from Figure 47 in the textbook for the case of control signal Ctrl1 being active by its error polynomial. Assume that the bus lines are completely reversed, i.e., b_{n-1} becomes b_0 etc. The error polynomial should be expressed in terms of input values to the block driving the bus.
 - c) Describe error type 10 by the error polynomial. Assume that when the both drivers are active the signals arithmetically add up (word-level quantities add up).
4. (Event-driven simulation – 20 points). Consider the circuit from Example 25. Replace AND gate with OR and vice-versa and show the following:
- a) Circuit diagram and timing diagram for the same input sequence as in Fig 25.a
 - b) Table with scheduled events and activity list for event-driven simulator

*All references are to the textbook by Radecka and Zilic. Other textbooks are not required for the completion of this assignment and in some instances have no equivalent description.